

CPE 166 Advance Logic Design

Harpreet Sidhu

Lab Section #3

Lab 3 Report

David Quintanilla

## Table of Contents

• Introduction .....	3
• Part 1 : (7,4) Hamming Code Generator .....	4- 11
○ Step 1 Parity Function .....	4
○ Step 2 Even Parity Bit of 2-bit Input Data .....	5-6
○ Step 3 (7,4) Hamming Code Generator .....	7 -11
• Part 2 : Pseudorandom Number Generator .....	12 - 14
○ Step 1 LFSR Design Review	
○ Step 2 LFSR Testbench Review for Fig 2. Circuit	
○ Step 3 LFSR Design and Testbench Simulation of Fig 1. Circuit .....	12 - 14
• Part 3 : Algorithmic State Machine (ASM) Charts .....	15 - 20
○ Step 3 Final Project Work.....	15 - 20
• Part 4: Stopwatch Design .....	21 - 36
○ Step 1 clkdiv block .....	21 - 23
○ Step 2 FSM block .....	23 - 27
○ Step 3 Watch block .....	27 - 32
○ Step 4 Final stopwatch block .....	33 - 36
• Conclusion .....	37

## Introduction

Lab 3 introduced a wide variety of topics including the introduction to Hamming Code, Linear Feedback Shift Registers and Algorithmic State Machines (ASM). In Part 1, I learned a basic understanding of Hamming Code. Consisting of bits and Parity bits, the key of Hamming code, is the use of extra parity bits to allow the correction of a single bit error. Furthermore, learning that an even parity bit is the bit added to the data block that ensures that the total number of bits in the message is even for error detection. Out of all the parts in Lab 3, Hamming Code was the one that stuck with me the most. Part 2 introduced the Linear Feedback Shift Register, which is a shift register whose input bit is the output of a linear logic function of two or more of its previous states. The LFSR was something I was very familiar with so Part 2 was fairly simple to follow along.

Moving along to Part 3, Algorithmic State Machines (ASM) were introduced and were to be written in VHDL. ASM's consisted of a State box, Optional decision box and a Optional conditional output box. Part 3 was quite challenging for me due to my lack of familiarity with VHDL, however the concepts of ASM were understood after a couple days practice. ASM were also a key for Part 4. The final part, Part 4 asked to design a Stop watch following a set of guidelines given in the procedures. Part 4 was by far the hardest part of the lab and required several attempts to finally have a complete running waveform.

## Part 1 : Hamming Code Generator

### Step 1 Parity Function

```
library ieee;

use ieee.std_logic_1164.all;

package MY_PACK is

function PARITY (D : std_logic_vector) -- declaration of function
return std_logic;

end MY_PACK;

package body MY_PACK is

function PARITY (D : std_logic_vector) -- implementation of function inside the
package body

return std_logic is

variable TMP : std_logic;

begin

    TMP := D(0);

    for J in 1 to D'high loop

        TMP := TMP xor D(J);

    end loop; -- works for any size of D

    return TMP;

end PARITY; -- even parity

end MY_PACK;
```

### Step 2 Even Parity Bit of 3-bit input Data (Verilog)

```
library ieee;
```

```

use ieee.std_logic_1164.all;
use work.MY_PACK.all;

entity PAR is
port( db: in std_logic_vector(2 downto 0);
      pb: out std_logic);
end PAR;

```

```

architecture ARCH of PAR is
begin
    pb <= PARITY(db);
end ARCH;

```

### **Step 2 Even Parity Bit of 3-bit input Data (Test Bench)**

```

library IEEE;
use IEEE.std_logic_1164.all;

entity PAR_tb is

end PAR_tb;

architecture Behavioral of PAR_tb is
    component PAR
        port( db: in std_logic_vector (2 downto 0) ;
              pb: out std_logic );
    end component;

```

```
signal db: std_logic_vector (2 downto 0) ;  
signal pb: std_logic;
```

```
begin
```

```
    uut: PAR port map(db => db, pb => pb);
```

```
    process begin
```

```
        db<="000";
```

```
        wait for 200 ns;
```

```
        db<="001";
```

```
        wait for 200 ns;
```

```
        db<="010";
```

```
        wait for 200 ns;
```

```
        db<="011";
```

```
        wait for 200 ns;
```

```
        db<="100";
```

```
        wait for 200 ns;
```

```
        db<="101";
```

```
        wait for 200 ns;
```

```
        db<="110";
```

```
        wait for 200 ns;
```


```
        db<="111";
```

```
        wait for 200 ns;
```

```
        wait;
```

```
    end process;
```

```
end Behavioral;
```

 **Wave Form (PAR)****Step 3 : (7, 4) Hamming Code Generator (Verilog)**

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
use work.MY_PACK.all;

entity hamming is

port( d3: in std_logic;
      d5: in std_logic;
      d6: in std_logic;
      d7: in std_logic;
      dout: out std_logic_vector(7 downto 1));

end hamming;

```

architecture behavioral of hamming is

begin

```
dout <= ((D7) & (D6) & (D5) & (PARITY(D7&D6&D5)) & (D3) &
(PARITY(D7&D6&D3)) & (PARITY(D7&D5&D3)));
```

end behavioral;

### **Test Bench**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity hamming\_tb is

end hamming\_tb;

architecture Behavioral of hamming\_tb is

component hamming

port( d3: in std\_logic;

d5: in std\_logic;

d6: in std\_logic;

d7: in std\_logic;

dout: out std\_logic\_vector(7 downto 1));

end component;



```

signal d3: std_logic;
signal d5: std_logic;
signal d6: std_logic;
signal d7: std_logic;
signal dout: std_logic_vector(7 downto 1);

```

```

begin

```

```

    uut: hamming port map( d3 => d3 , d5 => d5 , d6 => d6, d7 => d7 , dout => dout);

```

```

    process begin

```

```

        d7<='0';d6<='0'; d5<='0'; d3<='0';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='0'; d5<='0'; d3<='1';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='0'; d5<='1'; d3<='0';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='0'; d5<='1'; d3<='1';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='1'; d5<='0'; d3<='0';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='1'; d5<='0'; d3<='1';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='1'; d5<='1'; d3<='0';

```

```

        wait for 200 ns;

```

```

        d7<='0';d6<='1'; d5<='1'; d3<='1';

```

```

        wait for 200 ns;

```

```

        d7<='1';d6<='0'; d5<='0'; d3<='0';

```

```

        wait for 200 ns;


```

```
d7<='1';d6<='0'; d5<='0'; d3<='1';  
wait for 200 ns;  
d7<='1';d6<='0'; d5<='1'; d3<='0';  
wait for 200 ns;  
d7<='1';d6<='0'; d5<='1'; d3<='1';  
wait for 200 ns;  
d7<='1';d6<='1'; d5<='0'; d3<='0';  
wait for 200 ns;  
d7<='1';d6<='1'; d5<='0'; d3<='1';  
wait for 200 ns;  
d7<='1';d6<='1'; d5<='1'; d3<='0';  
wait for 200 ns;  
d7<='1';d6<='1'; d5<='1'; d3<='1';
```

```
end process;
```

```
end Behavioral;
```

Wave Form

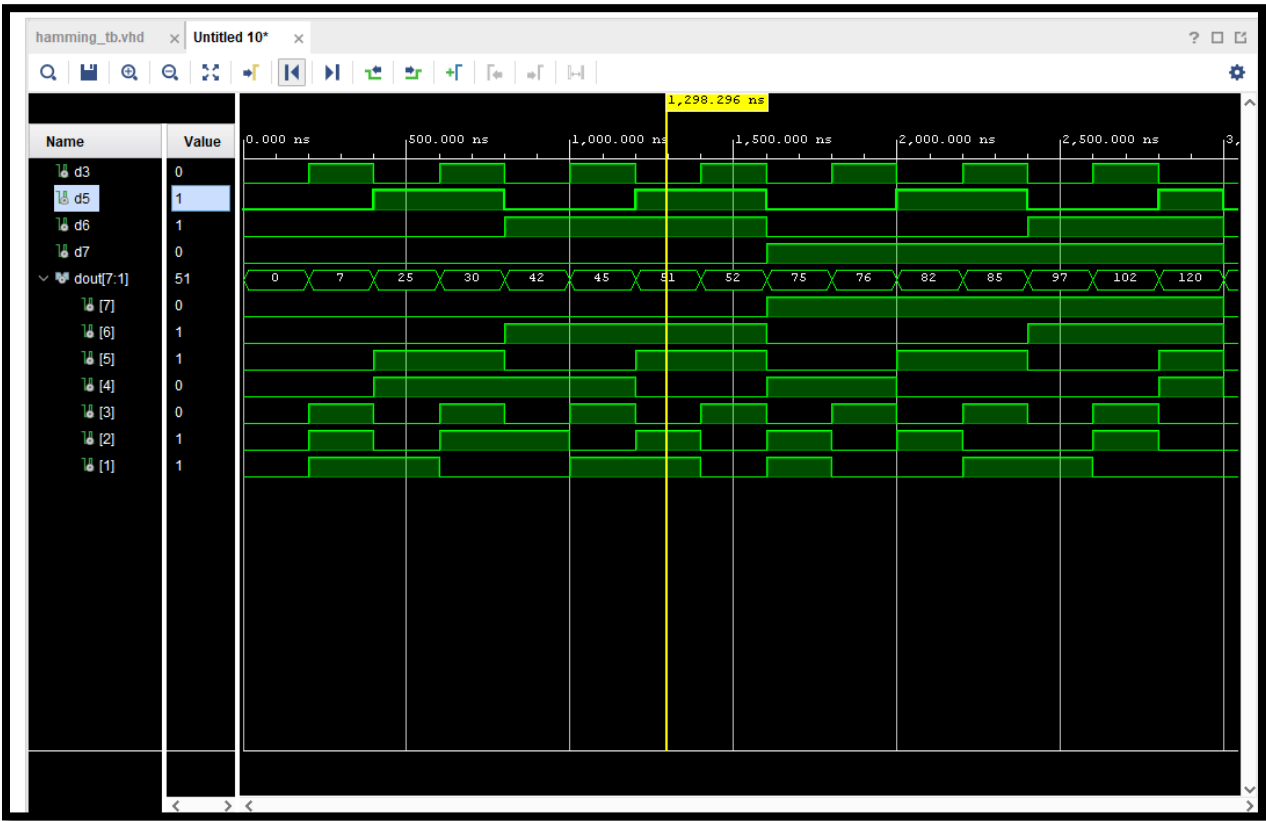

## Part 2 Pseudorandom Number Generator

### Step 1, 2, 3 LFSR Design (Verilog)

Library ieee;

Use ieee.std\_logic\_1164.all;

Entity LSFR is

Port ( reset, clk: in std\_logic;

Q: out std\_logic\_vector (4 downto 0) );

End LSFR;

Architecture beh of LSFR is

Signal m: std\_logic\_vector (4 downto 0);

Begin

Process(reset, clk)

Begin

If ( reset = '1') then

m <= ( 0=> '1', others =>'0'); --- value of “0001”

elsif (rising\_edge(clk) ) then

m(4 downto 1) <= m(3 downto 0)

m(0) <= m(2) xor m(3);

end if;

end process;

Q <= m;

end beh;

### **Step 1, 2, 3 LFSR Design (Test Bench)**

Library ieee;

Use ieee.std\_logic\_1164.all;

Entity LSFR\_tb is

End LSFR\_tb;

Architecture tb of LSFR\_tb is

signal clk, reset: std\_logic;

signal Q: std\_logic\_vector (4 downto 0);

component LSFR

Port ( reset, clk: in std\_logic;

Q: out std\_logic\_vector (4 downto 0) );

End component;

Begin

     uut: LSFR port map(reset, clk, Q);

    Process Begin

        Clk <= '0';

        Wait for 5 ns;

        Clk <= '1';

        Wait for 5 ns;

End process;

Process Begin

    Reset <= '1';

    Wait for 2 ns;

    Reset <= '0';


    Wait for 200ns;

    Wait;

End process;

End tb;

### Wave Form

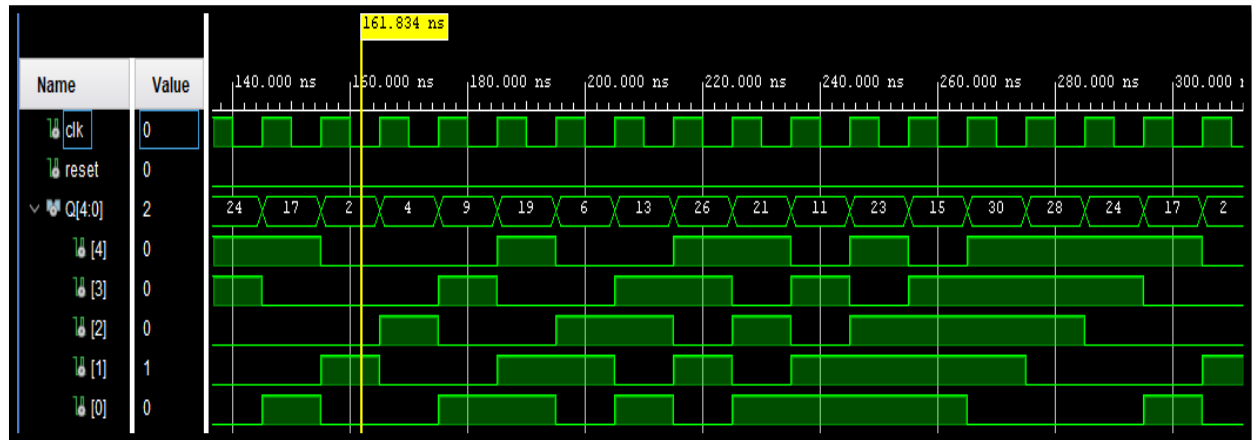

## Part 3: Algorithmic State Machine (ASM) Charts

- Steps 1 & 2 are review of ASM charts and code that we learned in class

### **Step 3. Final Project Work**

Library ieee;

Use ieee.std\_logic\_1164.all;

entity ASM is

port(

reset, clk, x: in std\_logic;

y1: out std\_logic;

y0, z: out std\_logic\_vector (1 downto 0);

ckcs, ckns: out std\_logic\_vector (1 downto 0)

);

end ASM;

architecture Behavioral of ASM is

constant S0: std\_logic\_vector(1 downto 0) := "00";

constant S1: std\_logic\_vector(1 downto 0) := "01";

constant S2: std\_logic\_vector(1 downto 0) := "10";

```
constant S3: std_logic_vector(1 downto 0) := "11";

signal cs, ns: std_logic_vector(1 downto 0);

begin

ckns <= ns;
ckcs <= cs;

process(reset, clk) begin

    if(reset = '1') then
        cs <= S0;
    elsif(rising_edge(clk)) then
        cs <= ns;
    end if;
end process;

process(cs, x) begin
    case(cs) is
        when S0 =>
            if(x = '1') then
                ns <= S1;
            else
                ns <= S0;
            end if;

        when S1 =>
            if(x = '1') then
                ns <= S1;
            else
```



```

        ns <= S2;
    end if;

    when S2 =>
        if(x = '1') then
            ns <= S1;
        else
            ns <= S3;
        end if;

    when S3 =>
        ns <= S0;
    when others =>
        ns <= S0;
    end case;
end process;

y1 <= '1' when (cs = S1) else '0';

y0(0) <= '1' when (cs = S2) else '0';

y0(1) <= '1' when (cs = S3) else '0';

z(0) <= '1' when (cs = S1) and (x = '1') else '0';

z(1) <= '1' when (cs = S2) and (x = '1') else '0';

end Behavioral;
```

**Step 3. Final Project Work (Test Bench)**

```
library IEEE;
```

```
use IEEE.std_logic_1164.ALL;
```

```
entity ASM_tb is
```

```
end ASM_tb;
```

```
architecture Behavioral of ASM_tb is
```

```
    component ASM
```

```
    port(
```

```
        reset, clk, x: in std_logic;
```

```
        y1: out std_logic;
```

```
        y0, z: out std_logic_vector (1 downto 0);
```

```
        ckcs, ckns: out std_logic_vector (1 downto 0)
```

```
    );
```

```
end component;
```

```
signal reset, clk, x, y1: std_logic;
```

```
signal y0, z: std_logic_vector (1 downto 0);
```

```
signal ckcs, ckns: std_logic_vector (1 downto 0);
```

```
begin
```

```
    uut: ASM port map(reset => reset, clk => clk, x => x, y1 => y1, y0 => y0, z => z, ckcs =>
    ckcs, ckns => ckns);
```

```
process begin
```

```
    clk <= '0';
```

```
    wait for 5 ns;
```

```
    clk <= '1';
```

```
    wait for 5 ns;
```

```
end process;
```

```
    x <= '1', '0' after 10 ns, '1' after 40 ns, '0' after 60 ns, '1' after 80ns, '0' after 120ns, '1' after  
160 ns, '0' after 200 ns, '1' after 300 ns, '0' after 350 ns;
```

```
process begin
```

```
    reset <= '1';
```

```
    wait for 2 ns;
```

```
    reset <= '0';
```


```
    wait for 200 ns;
```

```
    wait;
```

```
end process;
```

```
end Behavioral;
```

Wave Form

 

## Part 4 : Stopwatch Design

### Step 1: clkdiv block (Verilog)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity clkdiv is
```

```
port(clkin: in std_logic;  
      clkout: out std_logic := '0' );  
end clkdiv;
```

```
architecture Behavioral of clkdiv is  
    signal cnt : integer range 0 to 10 := 0;
```

```
begin  
    process(clkin) begin  
        if(rising_edge(clkin)) then  
            if(cnt = 10) then  
                cnt <= 0;  
                clkout <= '1';  
            elsif (cnt < 3) then  
                cnt <= cnt + 1;  
                clkout <= '1';  
            else  
                cnt <= cnt + 1;  
                clkout <= '0';  
            end if;  
        end if;  
    end process;
```

```

        end if;
    end if;
end process;
end Behavioral;

```

### **Step 1 clkdiv (Test Bench)**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity clkdiv_tb is
-- Port ( );
end clkdiv_tb;


architecture Behavioral of clkdiv_tb is
    component clkdiv
        port ( clkin : in std_logic;
              clkout : out std_logic );
    end component;
    signal clkin, clkout : std_logic := '0';
begin
    DUT : clkdiv
        port map(clkin=>clkin,clkout=>clkout);

    process begin
        wait for 10 ns;
        clkin <= not clkin;
    end process;

```

```
end Behavioral;
```

### WaveForm

 

### Step 2 : FSM Block

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity FSM is
```

```
    Port (clk, start, stop, reset: in std_logic;
```

```
          en: out std_logic);
```

```
end FSM;
```

```
architecture Behavioral of FSM is
```

```
    constant s0: std_logic_vector(1 downto 0) := "00";
```

```
    constant s1: std_logic_vector(1 downto 0) := "01";
```

```
signal cs, ns: std_logic_vector(1 downto 0);
```

```
begin
```

```
    process(reset, clk)
```

```
        begin
```

```
            if(reset = '1') then
```

```
                cs <= S0;
```

```
            elsif (rising_edge(clk)) then
```

```
                cs <= ns;
```

```
            end if;
```

```
        end process;
```

```
    process(cs, start, stop)
```

```
        begin
```

```
            case(cs) is
```

```
                when S0 => if (start='1') then
```

```
                    ns <= S1;
```

```
                else
```

```
                    ns <= S0;
```

```
                end if;
```



```

    when S1 => if (stop='1') then
        ns <= S0;
    else
        ns <= S1;
    end if;
    when others => ns <= S0;
end case;
end process;
en <= '1' when (cs = S1 and Start = '1') else '0';
end Behavioral;

```

### **Step 2 FSM Block (Test Bench)**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fsm_tb is
end fsm_tb;

architecture Behavioral of fsm_tb is
    component fsm
        port (clk, start, stop, reset: in std_logic;
              en: out std_logic);
    end component;
    signal clk, start, stop, reset, en: std_logic;
begin
    DUT: fsm port map(clk, start, stop, reset, en);
end Behavioral;

```

```
process
```

```
begin
```

```
    clk <= '0';
```

```
    wait for 1 ns;
```

```
    clk <= '1';
```

```
    wait for 1 ns;
```

```
end process;
```

```
process
```

```
begin
```

```
    start <= '0';
```

```
    stop <= '0';
```

```
    reset <= '1';
```

```
    wait for 10 ns;
```

```
    reset <= '0';
```

```
    stop <= '1';
```

```
    wait for 20 ns;
```

```
    stop <= '0';
```

```
    start <= '1';
```

```
    wait for 40 ns;
```

```
    start <= '0';
```


```
    stop <= '1';
```

```

        wait for 100 ns;
        wait;
    end process;
end Behavioral;

```

## Step 2 Wave Form

 

## Step 3 : Watch (Verilog)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

```

entity watch is

```

    Port (en, clk, reset: in std_logic;
          y0, y1, y2: out std_logic_vector(3 downto 0));
end watch;

```

architecture Behavioral of watch is

```
signal y0_reg: std_logic_vector(3 downto 0);  
signal y1_reg: std_logic_vector(3 downto 0);  
signal y2_reg: std_logic_vector(3 downto 0);
```

```
begin
```

```
    process(clk, reset)
```

```
    begin
```

```
        if(reset = '1') then
```

```
            y0_reg <= (others=>'0');
```

```
            y1_reg <= (others=>'0');
```

```
            y2_reg <= (others=>'0');
```

```
        elsif rising_edge(clk) then
```

```
            if(y0_reg = 9) then
```

```
                y0_reg <= (others=>'0');
```

```
            elsif(en = '1') then
```

```
                y0_reg <= y0_reg + 1;
```

```
            end if;
```

```
        if(y0_reg = 9) then
```

```
if(y1_reg = 9) then

    y1_reg <= (others=>'0');

else

    y1_reg <= y1_reg + 1;

end if;

end if;

if(y0_reg = 9 and y1_reg = 9) then

    if(y2_reg = 9) then

        y2_reg <= (others=>'0');

    else

        y2_reg <= y2_reg + 1;

    end if;

end if;

end if;

end process;
```

```

y0 <= y0_reg when (en = '1') or (reset = '1');
y1 <= y1_reg when (en = '1') or (reset = '1');
y2 <= y2_reg when (en = '1') or (reset = '1');

```

```

end Behavioral;

```

### **Step 3: Watch (Test Bench)**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity watch_tb is
end watch_tb;

architecture Behavioral of watch_tb is
    component watch
        port (en, clk, reset: in std_logic;
              y0, y1, y2: out std_logic_vector(3 downto 0));
    end component;
    signal en, clk, reset: std_logic;
    signal y0, y1, y2: std_logic_vector(3 downto 0);
    begin

        DUT: watch port map(en, clk, reset, y0, y1, y2);

    process

    begin

        clk <= '0';

```

```
wait for 1 ns;

clk <= '1';

wait for 1 ns;
end process;

process
begin

    en <= '0';

    reset <= '1';

    wait for 20 ns;

    en <= '1';

    wait for 20 ns;

    reset <= '1';

    wait for 20 ns;

    reset <= '0';

    wait for 20 ns;

    en <= '0';
```

```
wait for 20 ns;
```

```
en <= '1';
```

```
wait for 20 ns;
```


```
en <= '0';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

### Step 3 ( Wave Form )

 



**Step 4 Final Stopwatch (Verilog)**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

entity stopwatch is
    Port (start, stop, clk, reset: in std_logic;
          y0, y1, y2: out std_logic_vector(3 downto 0));
end stopwatch;

architecture Behavioral of stopwatch is

    signal en, clk2: std_logic;

    component clkdiv
        port (clkin: in std_logic;

              clkout: out std_logic);
    end component;

    component fsm
        port (clk, start, stop, reset: in std_logic;
```

```

        en: out std_logic);

end component;

component watch

    port (en, clk, reset: in std_logic;
          y0, y1, y2: out std_logic_vector(3 downto 0));

end component;

begin
    g1: clkdiv port map(clkin => clk, clkout => clk2);
    g2: fsm port map(clk => clk2, start => start, stop => stop, reset => reset, en => en);
    g3: watch port map(en => en, clk => clk2, reset => reset, y0 => y0, y1 => y1, y2 => y2);

end Behavioral;

```

#### **Step 4 Final Stopwatch (Test Bench)**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity stopwatch_tb is
end stopwatch_tb;

architecture Behavioral of stopwatch_tb is
    component stopwatch
        port (start, stop, clk, reset: in std_logic;
              y0, y1, y2: out std_logic_vector(3 downto 0));
    end component;

```

```
end component;
```

```
signal start, stop, clk, reset: std_logic;
```

```
signal y0, y1, y2: std_logic_vector(3 downto 0);
```

```
begin
```

```
    DUT: stopwatch port map(start, stop, clk, reset, y0, y1, y2);
```

```
process
```

```
begin
```

```
    clk <= '0';
```

```
    wait for 1 ns;
```

```
    clk <= '1';
```

```
    wait for 1 ns;
```

```
end process;
```

```
process
```

```
begin
```

```
    start <= '0';
```

```
    stop <= '0';
```

```
    reset <= '1';
```

```
    wait for 20 ns;
```

```
    reset <= '0';
```

```
    stop <= '1';
```

```
    wait for 20 ns;
```



## **Conclusion**

Lab 3 had its own set of challenges that were both familiar and new. One of the biggest lessons learned in this lab was understanding VHDL in a deeper context and the concept of Hamming Code. Some parts of this lab overlap with previous labs such as the clk divider and FSM. A key concept of lab 3 that I took away was “port mapping”. Although this is not a new concept to me, I really understood the concept of porting in lab 3.