


# CSUS CPE166 Dummy Exercise

Student Name: David Quintanilla

You need to upload the solution in multi-page PDF or WORD file format on the canvas course website.

You must write down your name on your solution sheets.

 - Complete the Verilog HDL design for the circuit below.



```

module ex1 ( M, N, P, Y );
input  M, N, P ;
output Y[1:0] ;
wire  a, b, c, d, e, f ;
assign a = ~(M & N) ;
assign b = ~(M & N) ;
assign c = B & E ;
assign d = B & ~A ;
assign e = ~P ;
assign f = ~E ;
assign Y[1] = ~(A | C) ;
assign Y[0] = D ^ E ;
endmodule
    
```

2. Write a testbench for the above circuit. You must generate testing cases for all possible values of M, N, and P.

```
`timescale 1ns/1ps
```

```
module ex1_tb();
```

```
  Reg MNP;
```

```
  wire [1:0] Y
```

```
  ex1 uut(.m(M), .N(N), .P(P));
```

```
  Initial begin
```

```
    M=0; N=0; P=0;
```

```
    #5
```

```
    M=0; N=0; P=1;
```

```
    #5
```

```
    M=0; N=1; P=0;
```

```
    #5
```

```
    M=0; N=1; P=1;
```

```
    #5
```

```
    M=1; N=0; P=0;
```

```
    #5
```

```
    M=1; N=0; P=1;
```

```
    #5
```

```
    M=1; N=1; P=0;
```

```
    #5
```

```
    M=1; N=1; P=1;
```

```
    #5
```

```
    M=0; N=0; P=0;
```

```
  end
```

```
  initial $monitor($time, "M=%b, N=%b, P=%b" M, N, P);
```


```
end module
```

3. Design a counter circuit in Verilog. The counter counts from 0 to 220 and then repeats.

```
module counter();  
    integer;  
  
    initial begin  
        where (1'b0) begin  
            for(j=0; j <= 220; j+1)  
                #10 display("counter = %d", j);  
            end  
        end  
    end  
end
```

endmodule

 4. Design the following circuit in Verilog.



```

module ex4 ( D, clk, M, Y);
    input D, clk;
    output M, Y;
    wire (w, p, q);

    assign w = (~D) & q;
    assign q = (p & q);
    assign p = q;

    always @ (posedge clk)
        if
  
```

5. Write a testbench for the circuit in the problem 4.

```
module ex4_tb;
```

```
    module ex4_tb;
```

```
        reg d, clk
```

```
        wire m, y;
```

```
        ex4(d, clk, m, y)
```

```
        initial clk = 1'b0
```

```
        always #6 clk = ~clk;
```

```
        initial
```

```
        begin
```

```
            d = 1'b0;
```

```
            #14 d = 1'b1;
```

```
            #5 d = 1'b0;
```

```
            #6 d = 1'b1;
```

```
            #16 d = 1'b0;
```

```
            #10 d = 1'b1;
```

```
            #12 d = 1'b1;
```

```
            #10 d = 1'b0;
```

```
            #18 d = 1'b1;
```

```
            #10 d = 1'b0;
```

```
            #10 d = 1'b0;
```

```
            #10 $stop;
```

```
        end
```

```
        initial $monitor($time, "d=%d, clk=%d, m=%d, y=%d", d, clk, m, y);
```

```
    endmodule
```